

# ELECTRIC CIRCUITS

## TWO CRUCIAL IDEAS

① VOLTAGE = DIFFERENCE IN  
ELECTRIC POTENTIAL

② CURRENT = FLOW OF ELECTRIC  
CHARGE

## CURRENT


SYMBOL  $I$

UNITS: AMPS (A),  $1A = 1C/s$

## MECHANICAL ANALOGY

VOLTAGE IS LIKE PRESSURE

CURRENT IS LIKE FLOW RATE

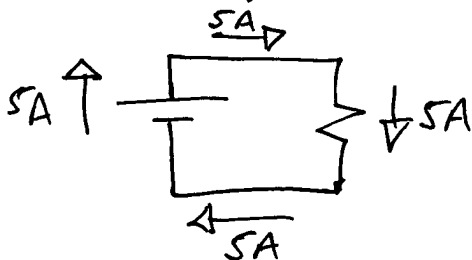

CURRENT DOESN'T GET USED UP.

# CIRCUITS ELEMENTS


- WIRES
- RESISTORS
- BATTERIES

## WIRES

- WIRES ARE MADE OF METAL (LIKE COPPER)
- METALS HAVE FREE ELECTRONS THAT CAN MOVE EASILY
- OUR WIRES ARE MODELLED BY PERFECT CONDUCTORS
- PERFECT CONDUCTORS HAVE  $\vec{E} = 0$  INSIDE.
- A PERFECT CONDUCTOR HAS THE SAME ELECTRIC POTENTIAL AT ALL POINTS.  
( $V$  IS UNIFORM.)
- EACH WIRE IN A CIRCUIT CAN BE ASSIGNED A SINGLE VALUE OF ELECTRIC POTENTIAL.
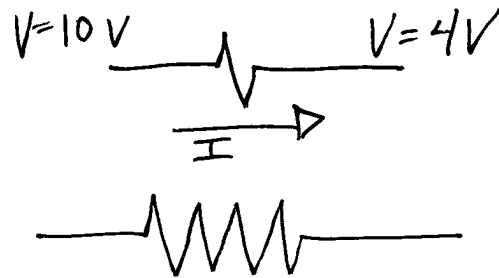
# RESISTORS

- RESISTORS ARE THINGS THAT "USE" ELECTRICITY.
- IN A LINEAR RESISTOR, THE VOLTAGE ACROSS THE RESISTOR IS PROPORTIONAL TO THE CURRENT THROUGH THE RESISTOR.



- LINEAR RESISTORS OBEY OHM'S LAW

$$V = IR$$

An arrow points from the text "VOLTAGE ACROSS RESISTOR" to the  $V$  in the equation. Below this text is the note "(6V IN OUR EXAMPLE)".  
 An arrow points from the text "CURRENT THROUGH RESISTOR" to the  $I$  in the equation.  
 An arrow points from the text "RESISTANCE" to the  $R$  in the equation.

- RESISTANCE IS MEASURED IN OHMS ( $\Omega$ )  
 $1\Omega = 1V/1A$



# BATTERIES


- BATTERIES HAVE A VOLTAGE RATING
- IDEAL BATTERIES CAN SUPPLY ANY AMOUNT OF CURRENT.

WARNING: REMEMBER TO USE IDEAS OF VOLTAGE AND ELECTRIC POTENTIAL.



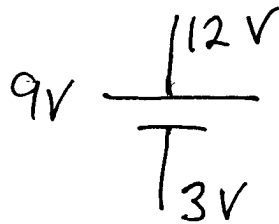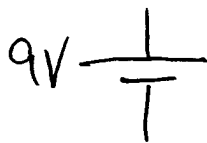- A BATTERY ENFORCES A DIFFERENCE OF ELECTRIC POTENTIAL




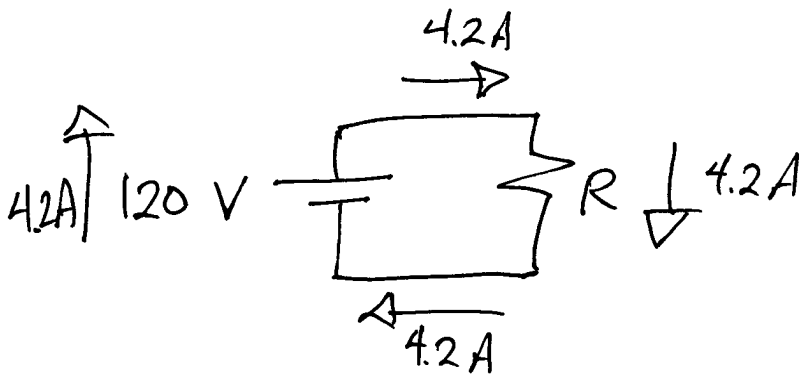

5
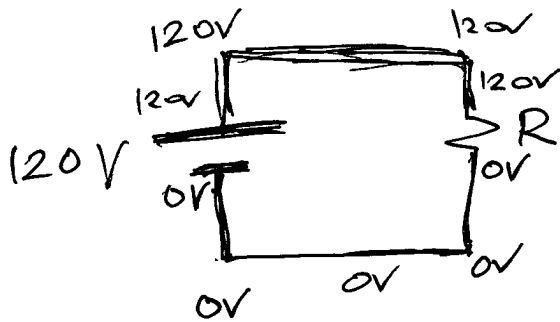
## CIRCUIT ANALYSIS TECHNIQUE #1


- LABEL THE WIRES WITH ELECTRIC POTENTIALS
  - CHOOSE ONE WIRE TO HAVE  $V=0V$ .
  - LABEL AS MANY WIRES AS YOU CAN WITH NUMERICAL ELECTRIC POTENTIALS.
  - LABEL REMAINING WIRES WITH VARIABLES ( $V_A, V_B$ , etc.)



$$V = IR$$

$$(120V - 0V) = (4.2A)R$$

$$R = \frac{120V}{4.2A} = 28.5 \Omega$$

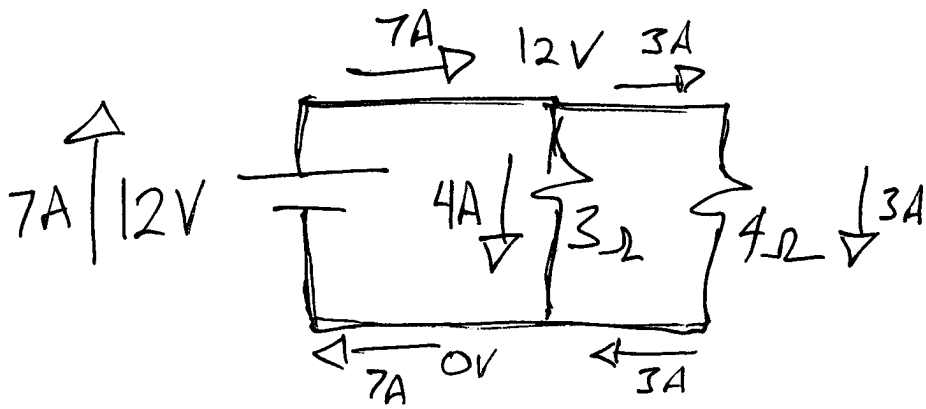

$$(12V - 0V) = I_{3\Omega} (3\Omega)$$

$$I_{3\Omega} = 4A$$

$$(12V - 0V) = I_{4\Omega} (4\Omega)$$

$$I_{4\Omega} = 3A$$

CIRCUIT ANALYSIS TECHNIQUE #2:

KIRCHHOFF'S ~~VOLTA~~ CURRENT LAW

CURRENT FLOWING INTO A JUNCTION  
EQUALS THE CURRENT FLOWING OUT.