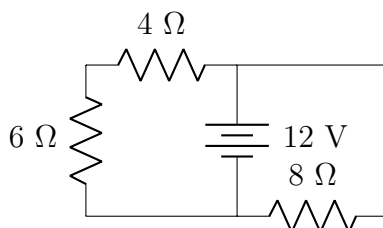


Yet More Circuit Problems


Physics 104

Analyze the circuit below. Give the voltage across and the current through each circuit element listed in the box provided.



	Voltage across	with high potential on which side? (left, right, top, bottom)	Current through	with current flowing toward what direction? (left, right, up,down)
4 Ω				
6 Ω				

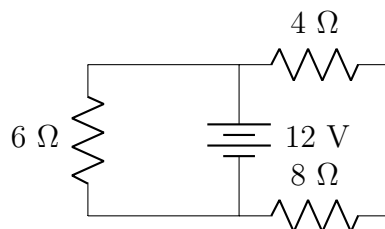Analyze the circuit below. Give the voltage across and the current through each circuit element listed in the box provided.



	Voltage across	with high potential on which side? (left, right, top, bottom)	Current through	with current flowing toward what direction? (left, right, up,down)
4 Ω				
6 Ω				