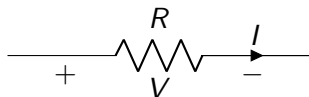


# Circuit Theory

Scott N. Walck

November 17, 2021


A resistor satisfies Ohm's law.



$$V = IR$$

- ▶  $V$  is the voltage across the resistor. The  $+$  and  $-$  mean that if  $V > 0$  then the electric potential is higher on the left. If  $V < 0$ , then the electric potential is higher on the right.
- ▶  $I$  is the current through the resistor. If  $I > 0$ , then (positive) current flows to the right. If  $I < 0$ , then current flows to the left.
- ▶ If the arrow for  $I$  is to the right, then the  $+$  for  $V$  must be on the left. Otherwise  $V = IR$  fails and needs a minus sign, which we don't want.

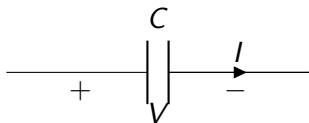A capacitor satisfies some other equations.




$$Q = CV$$

$$I = \frac{dQ}{dt}$$

$$I = C \frac{dV}{dt}$$


- ▶ The + and - mean that if  $V > 0$  then the electric potential is higher on the left. If  $V < 0$ , then the electric potential is higher on the right. (Same meaning as for a resistor.)
- ▶ If  $I > 0$ , then (positive) current flows to the right. If  $I < 0$ , then current flows to the left. (Same meaning as for a resistor.)
- ▶ If the arrow for  $I$  is to the right, then the + for  $V$  must be on the left. (Same as for a resistor.)

A battery is a constant voltage source.

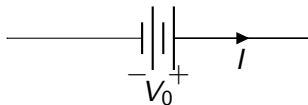

- ▶ We assume  $V_0 > 0$ . Electric potential is higher at the long bar.
- ▶ If  $I > 0$ , the battery is supplying power to the rest of the circuit. If  $I < 0$ , the battery is being recharged.

## A circuit

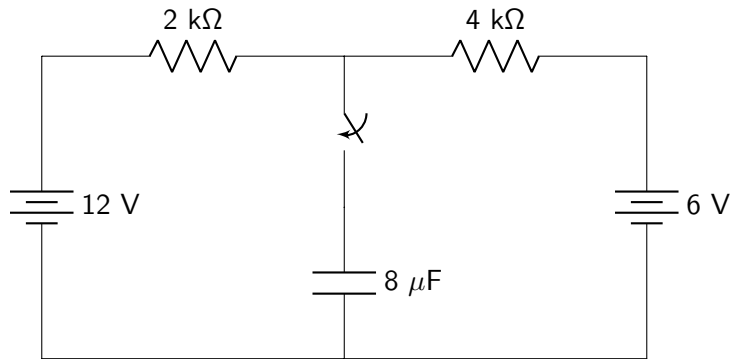

## Step 1: Label voltages and currents

